



# 模块 5


讲解：电池和电压调节


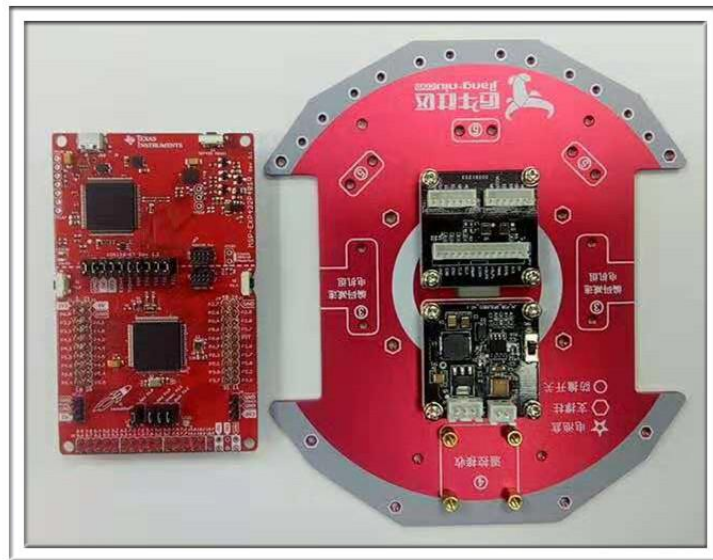
## 电池和电压调节

在本模块中您将学会：

- 电源 - 电池
  - 电压, V (伏特)
  - 电流, I (安培)
  - 功率, E (焦耳)
- 电压调节 (恒压)
  - 目的
  - 型号
  - 电路
- 性能测量 (实验)
  - 监测电池电压, 电流, 存储
  - 电压调节 (直流电压表)
  - 噪声 (交流电压表, 示波器)



电机驱动器和供电板为 TI Launchpad 开发板供电




# 功率和能量

## 功率来源

- 120/220 VAC（交流） 50/60 Hz
  - 需要AC到DC转换器
  - 需要一个稳压器
- 直流电源（USB上+ 5V，汽车上使用+ 12V）
  - 用于为TI的Launchpad（5V）供电的USB电源
- 电池
  - 需要自动驾驶机器人
  - 给TI的Launchpad，电机，传感器供电
  - 电压，能量，大小，重量
  - 需要稳压器以获得恒定电压
- 能量收集就像太阳能或电磁场一样收取

$$\text{Power} = V \cdot I \text{ (watts)}$$
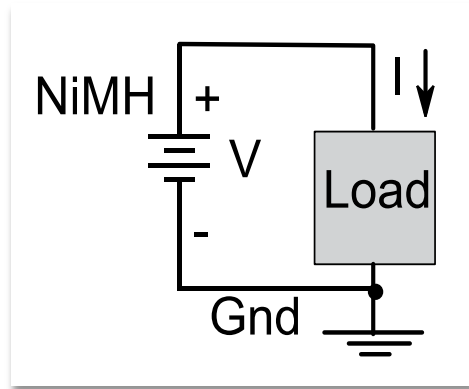
$$\text{Energy} = V \cdot I \cdot \text{time (Joules)}$$





# 功率预算

## 电池供电的嵌入式系统

- 功率预算=>电池寿命  
平均电流<储能/寿命

- 节能:


降低电压, 睡眠模式, 时钟, CPU,



TI Launchpad MSP432 低功耗MCU

$$\text{Energy} = V * I * \text{time}$$

$$\text{Storage} = I * \text{time (amp-hr)}$$

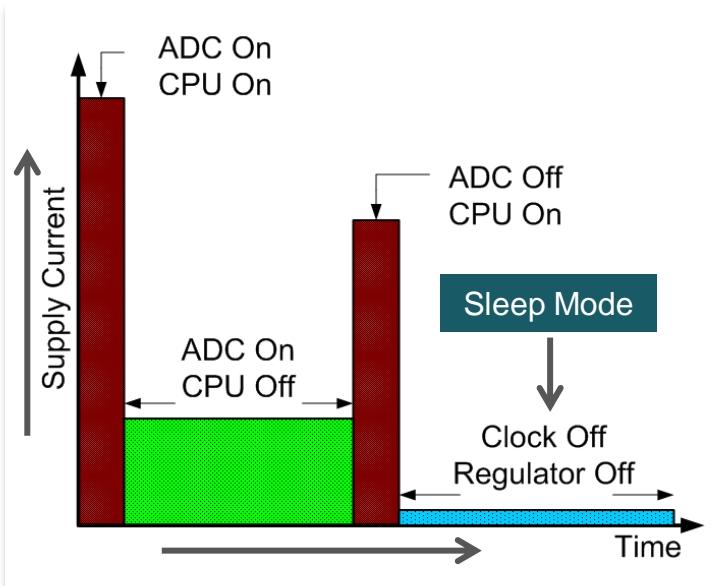

MSP432 : 在不同模式下供电



# 电池



## 电池的类型

- 不可充电
  - 重型电池 (Heavy duty)
  - 碱性电池 (Alkaline)
  - 铅酸电池 (Lead-acid)
  - 锂电池 (Lithium)
  
- 可充电的
  - 镍镉电池 (NiCad)
  - 镍氢电池 (NiMH)
  - 锂离子电池 (Li-ion)
  - 超级电容 (Supercap)

$$\text{Energy} = V * I * \text{time}$$

$$\text{Storage} = I * \text{time (amp-hr)}$$

Battery内部

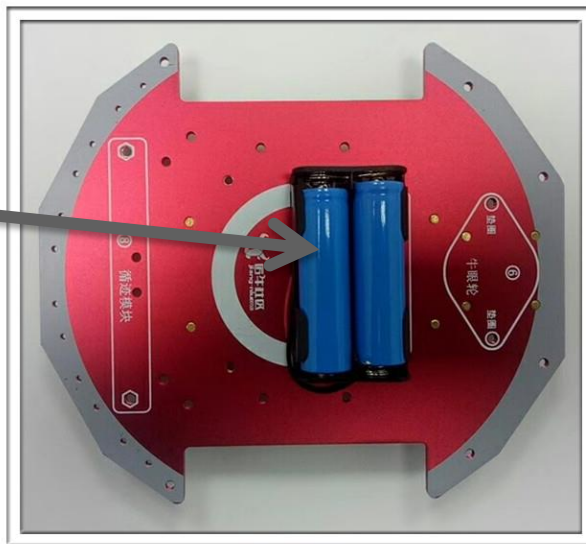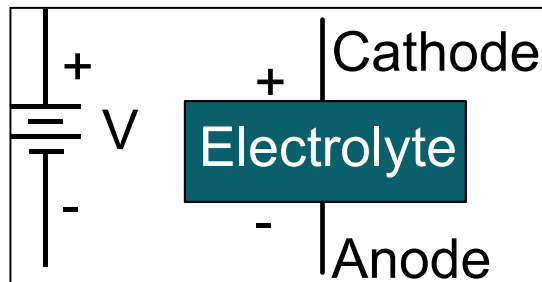



# 电池

## AA型电池

$$\begin{aligned} \text{Energy Storage} &= V * I * \text{time} \\ &= I * \text{time (amp-hr)} \end{aligned}$$

电池	电压 (V)	容量 (Ah)	类型
碱性电池	1.5	2	不可充电
锂电池	1.5	3	不可充电
镍镉电池	1.2	1.2	可充电
镍氢电池	1.2	1.8	可充电
锂离子电池	3.6	1.9	可充电

大多数能量用于相同尺寸的电池

以0.5A运行，您的机器人将运行3.6小时


$$\begin{aligned} t_{\text{life}} &= \text{Energy Storage} / I \\ &= 1.8 / 0.5 = 3.6 \text{ hr (NiMH)} \end{aligned}$$



## 使用线性稳压器进行电压调节
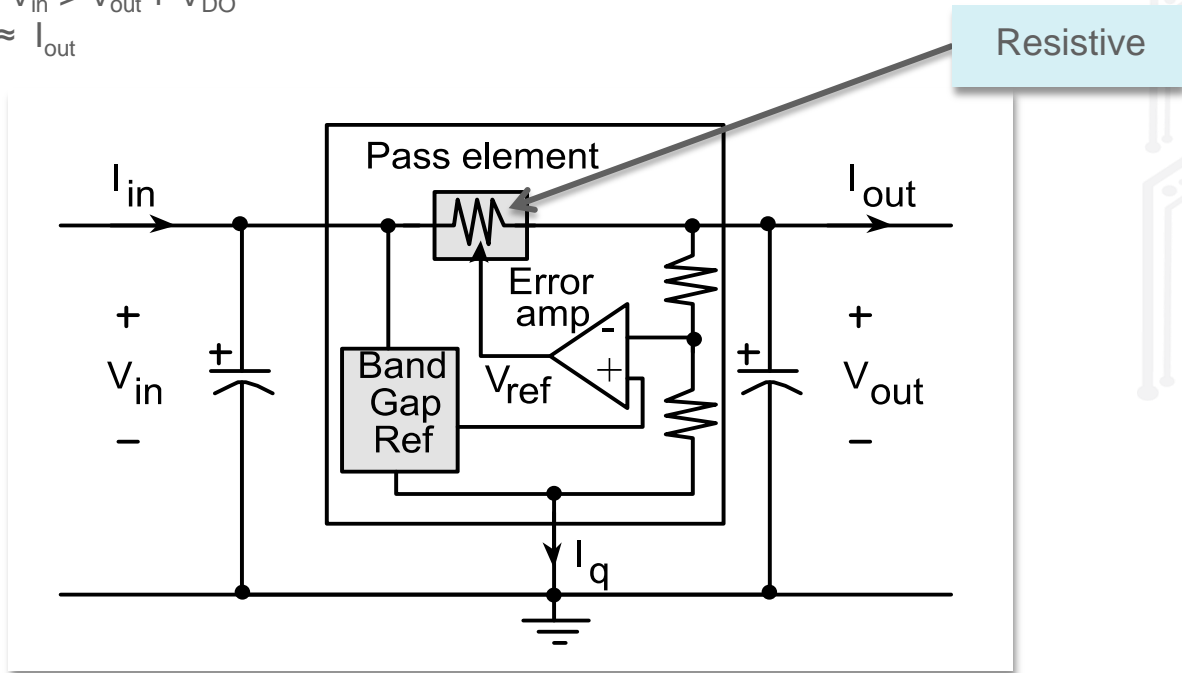
### 性能

- 产生恒定的输出电压 $V_{out}$ ，用于改变输入电压 $V_{in}$ 和负载 $I_{out}$
- Dropout voltage（压差电压）， $V_{in} > V_{out} + V_{DO}$
- 效率低（耗散更多功率）， $I_{in} \approx I_{out}$
- 低噪声



输入功率 - 输出功率 =  $7.2\text{ V} \times 100\text{ mA} - 5\text{ V} \times 100\text{ mA} = 0.22\text{ W}$  功率损耗!




## 使用线性稳压器进行电压调节
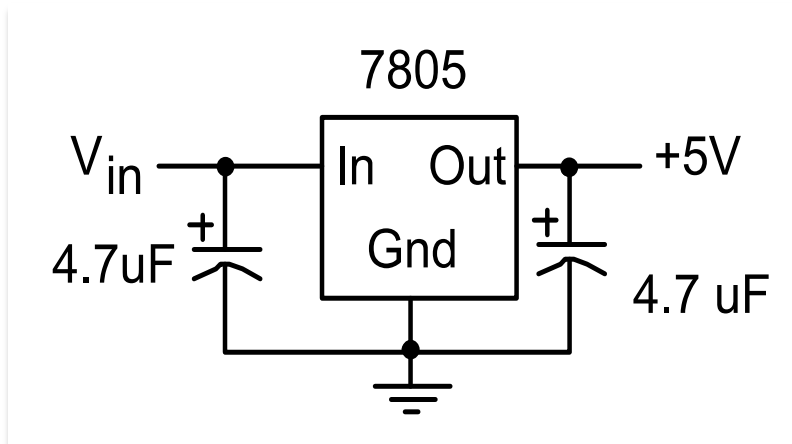
### 示例 +5V 稳压器

参数:

- $V_{in} > 7V$  ( $V_{DO} = 2V$ )
- $I_{out} < 1$  amp



如果您没有匠牛的电机驱动器供电板，请自行搭建此电路。

WEBENCH®是德州仪器（TI）的免费设计工具，您可以使用它来设计电源电路吗？

<http://www.ti.com.cn/zh-cn/tools-software/design-center/webench-power-designer.html>





# 使用开关稳压器进行电压调节

## 性能

- Buck: 降压 ( $V_{in} > V_{out}$ )
- Boost: 升压 ( $V_{in} < V_{out}$ )
- Buck-boost: 降压-升压
- 开关噪声




Power In  $\approx$  Power Out

$$V_{in} * I_{in} \approx V_{out} * I_{out}$$

$$\text{Efficiency} = (V_{out} * I_{out}) / (V_{in} * I_{in})$$


Or  $P_{out} / P_{in}$

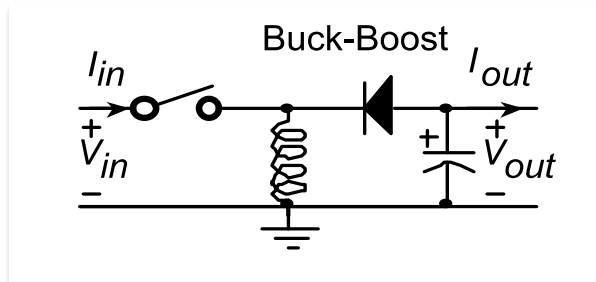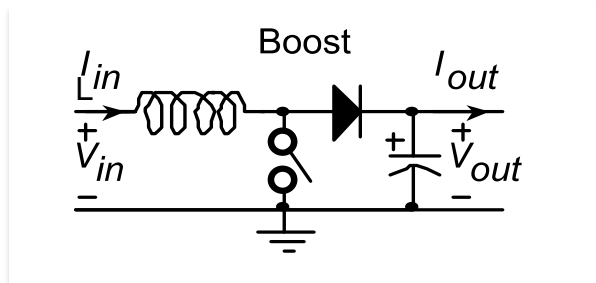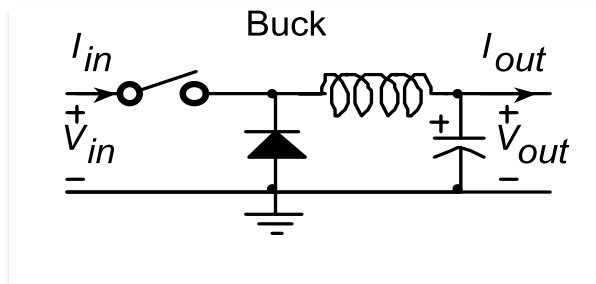要了解有关稳压器的更多信息，请访问 [ti.com/PMLK](https://www.ti.com/PMLK)






# 开关稳压器电路：一个例子

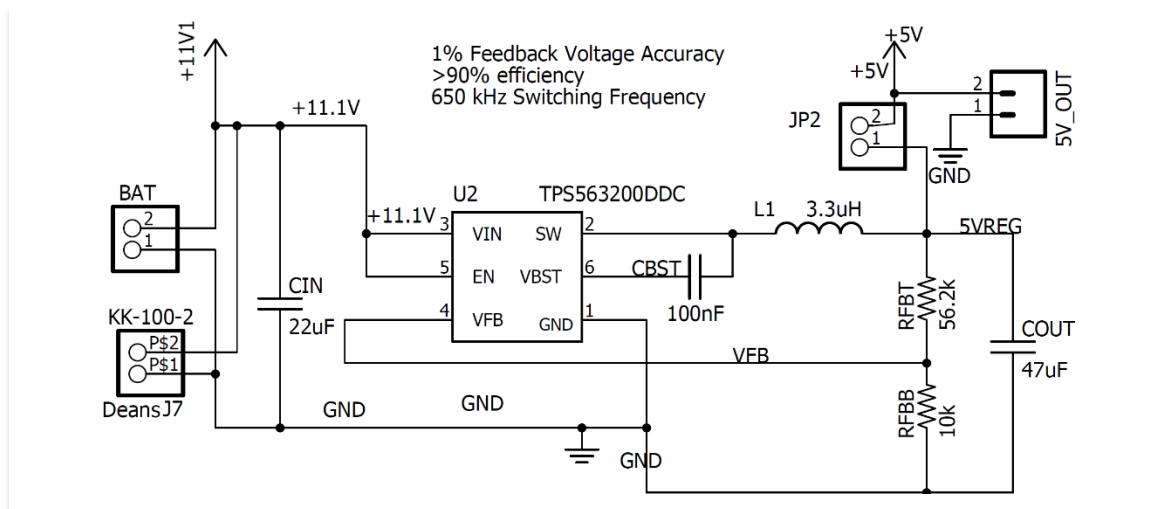

**警告：**  
注意不要将稳压器输出端的导线连接到地。！！

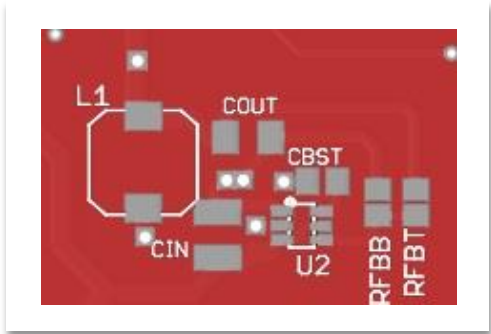

采用TI TPS563200 17V输入，2 A同步降压稳压器的开关稳压器的原理图和PCB

电机驱动器和配电板（来自实验）使用类似的调节器




## 开关稳压器电路：一个例子

- 3.3V, 5V, 12V和可调输出版本
- 降压（降压）开关稳压器
- 提供TO-220和TO-263封装
- 确保负载电流输出3A的版本
- 仅需要4个外部组件
- 150 kHz固定频率内部振荡器
- 高效率
- 热关断和限流保护

这些功能提供电路保护




TO-220-5 package

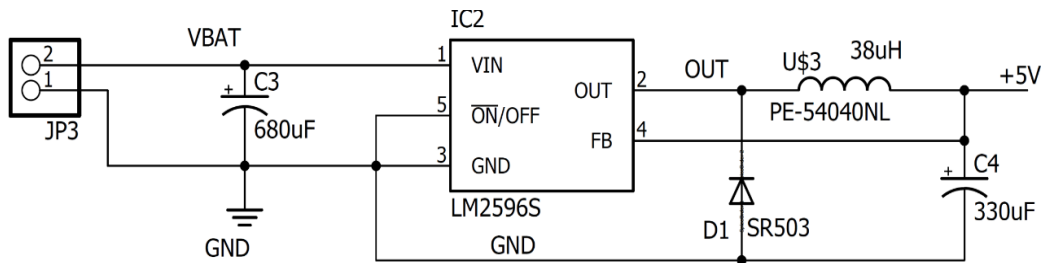

如果您没有匠牛的电机驱动器配电板或使用7805，请构建此电路。有关电源设计的更多信息，请访问 <http://www.ti.com/tool/lm2596s-adjev>

# 采用TI LM2596的开关稳压器电路板

- LM2596T-5.0
- 所有通孔部件
- 已验证电路

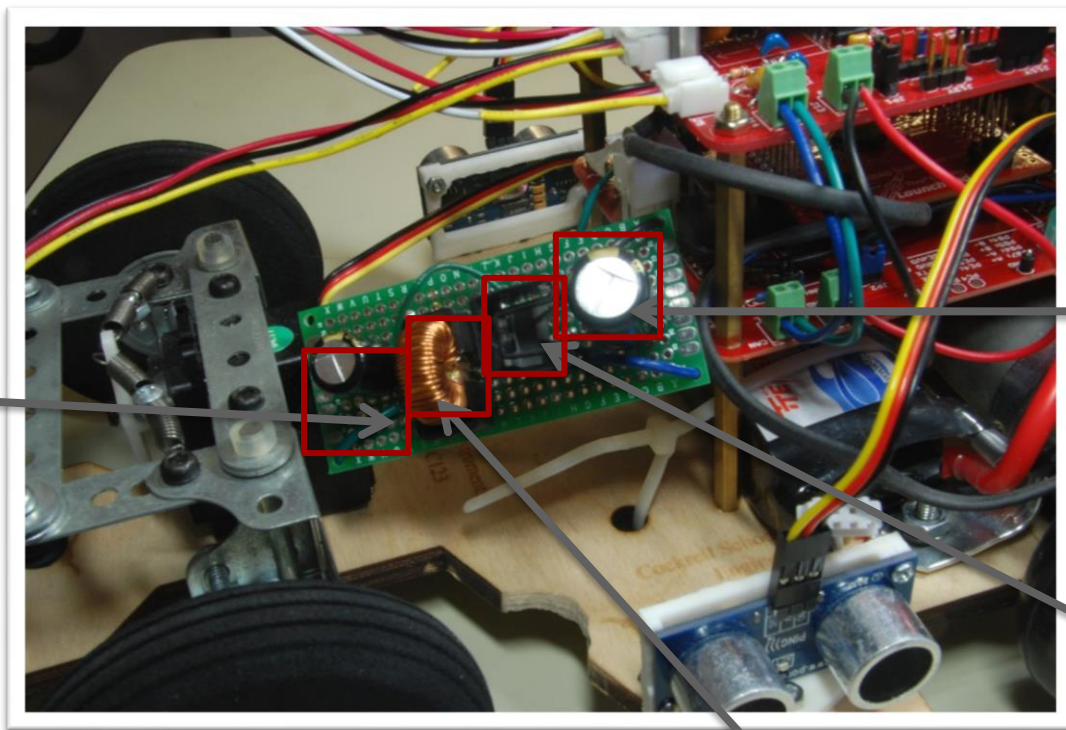

Cin

标准输出

LM2596T

电感


如果您没有匠牛的电机驱动器配电板，请构建此电路。



# 电池和电压调节
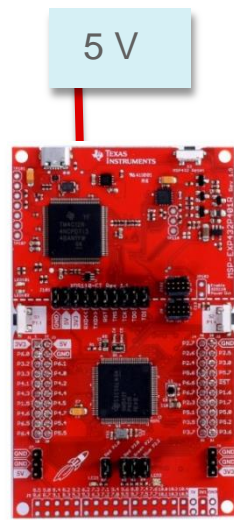
## 总结

- 电源 - 电池
  - 可充电和不可充电
  - 功率预算和电池容量
- 电压调节 - 线性稳压器
  - 低噪声
  - 耗散功率 =  $(V_{in} - V_{out}) * I_{out}$
  - 压差,  $V_{in} > V_{out} + V_{do}$
- 电压调节 - 开关稳压器
  - 更大的压降
  - 可升压
  - 高效率



Power =  $V * I$   
Energy =  $V * I * \text{time}$   
Energy Storage =  $I * \text{time}$   
Power Budget:  
Average Current <  $\text{Energy Storage} / t_{life}$

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2018, Texas Instruments Incorporated